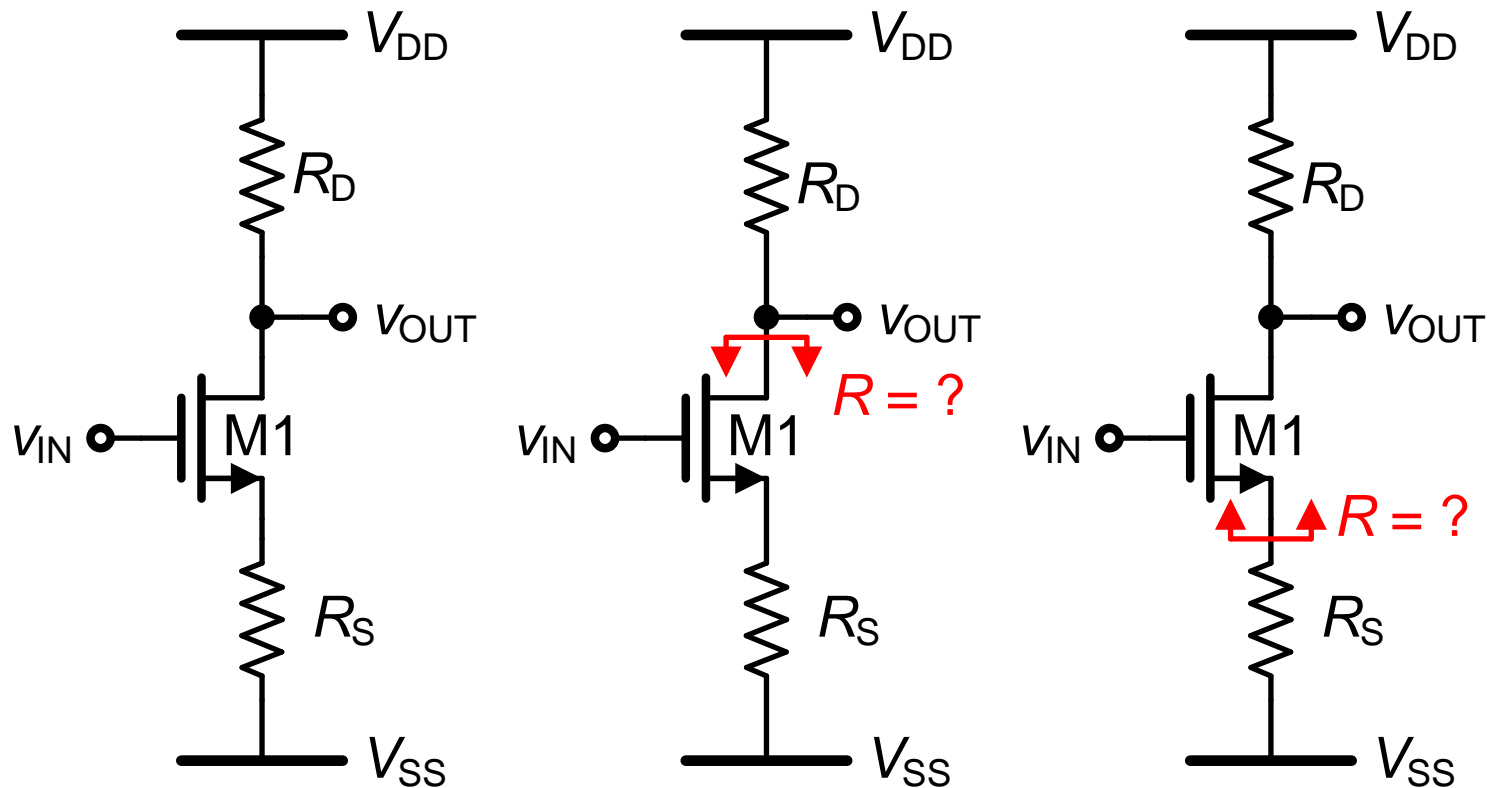


Equivalent Resistance



M1 is in the saturation zone.

Conclusion



Seen from Drain:

$$R = r_o + R_S + g_m r_o R_S$$

If $g_m R_S \gg 1$,

$$R \approx g_m r_o R_S$$

If $g_m R_S \ll 1$,

$$R \approx r_o$$

Seen from Source:

$$R = [(1/g_m) || r_o](1 + R_D/r_o)$$

If $R_D \gg r_o$,

$$R \approx R_D / (g_m r_o)$$

If $R_S \ll r_o$,

$$R \approx 1/g_m$$

DC Gain




Hints for gain calculation:

First, find the equivalent transconductance;

Second, find the output resistance;

Third, find their multiplication.

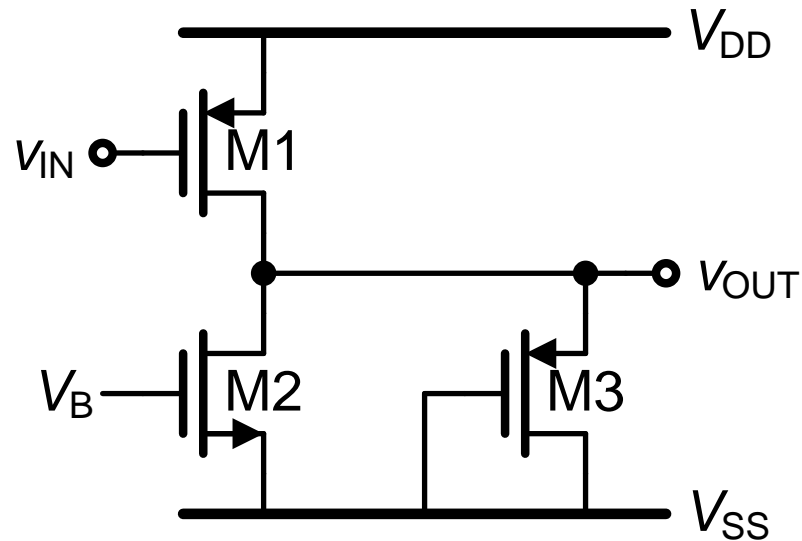


M1, M2, M3 are in the saturation zone.

Pole




M1 is in the saturation zone, r_o is very large, $R_D \ll r_o$.

1. DC gain?
2. Poles?

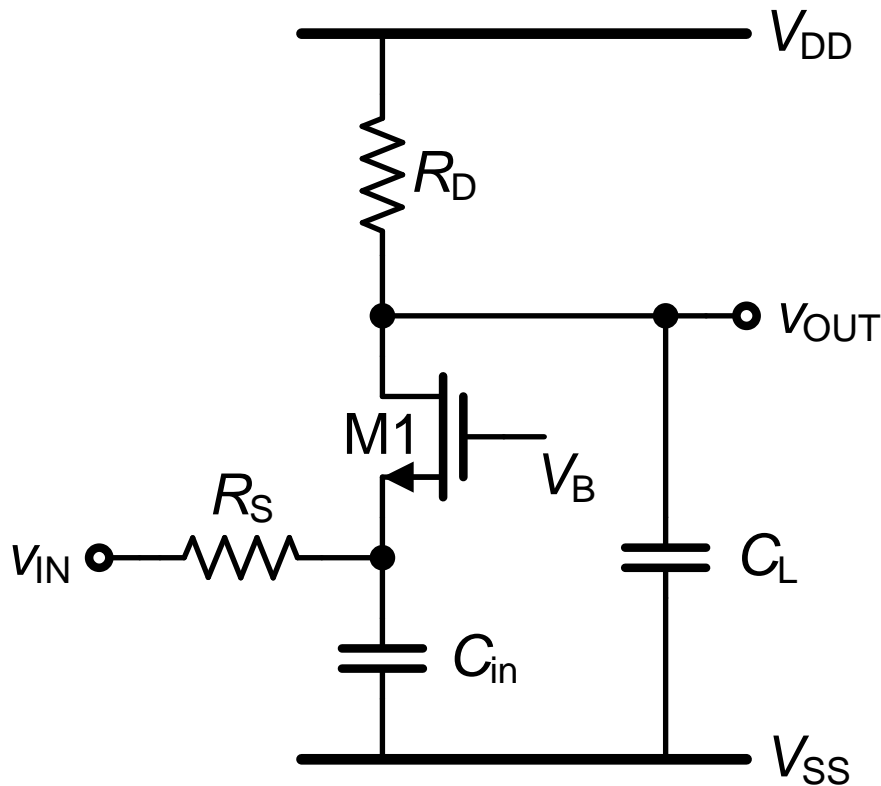


Frequency Response

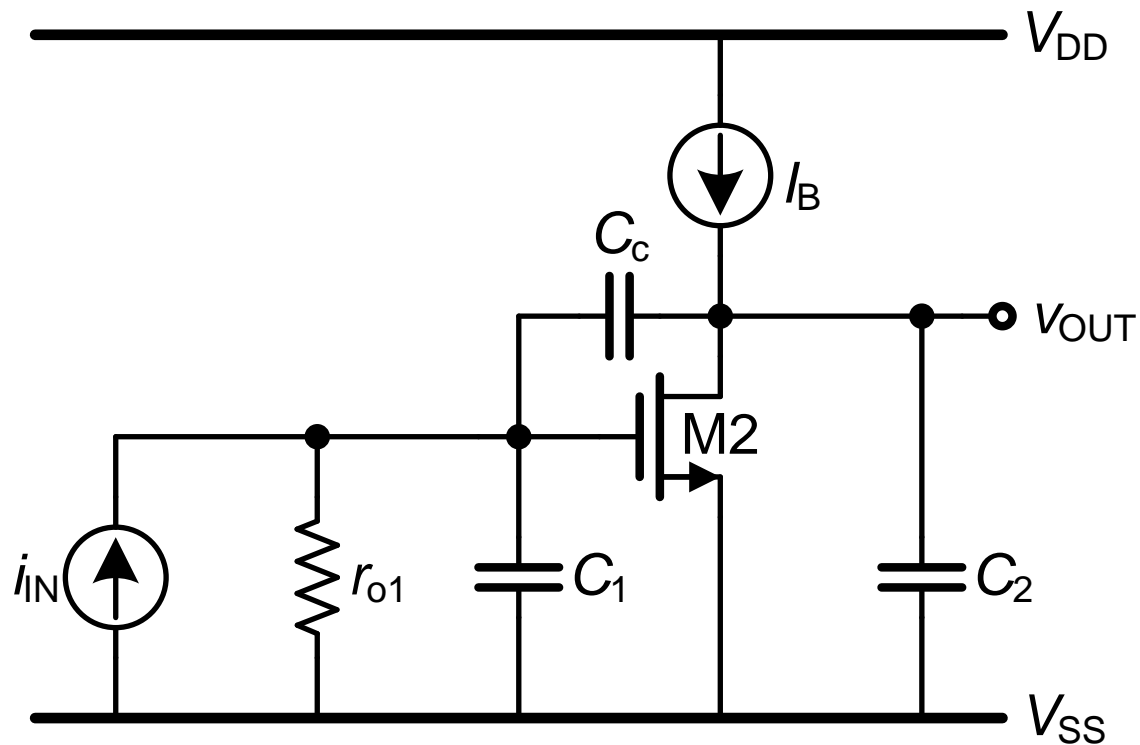

$M2$ is in the saturation zone.

Example

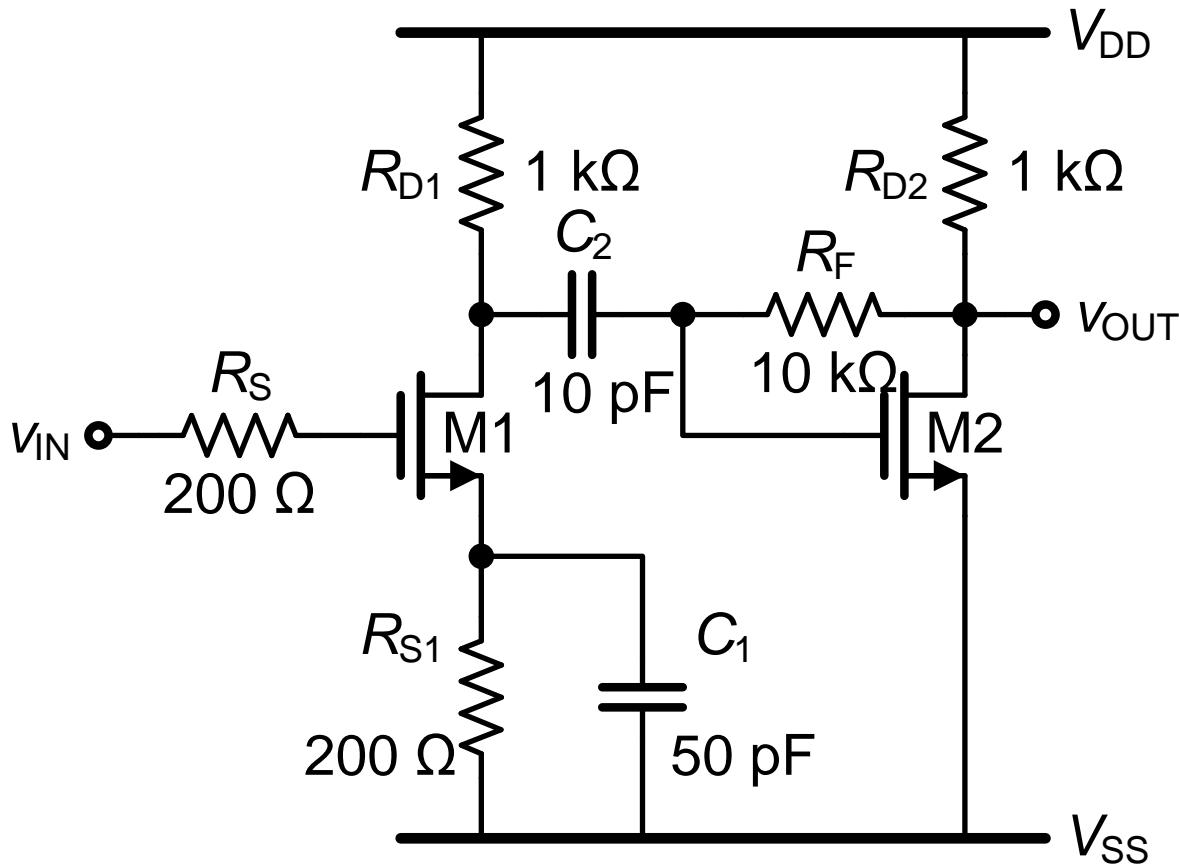

M1, M2 saturated
 $1/g_{m1} = 1/g_{m2} = 150 \Omega$
 $\lambda_1 = \lambda_2 = 0 \text{ V}^{-1}$
 $C_{gs1} = C_{gs2} = 250 \text{ fF}$
 $C_{gd1} = C_{gd2} = 80 \text{ fF}$
 $C_{db1} = C_{db2} = 100 \text{ fF}$
Find all the poles.



Thank you
for
your attention!